


Macro Identification

Prompt:

You are a professional analog circuit engineer. Please identify the type and function of this circuit diagram and reply in the following format:

Type:

Function:

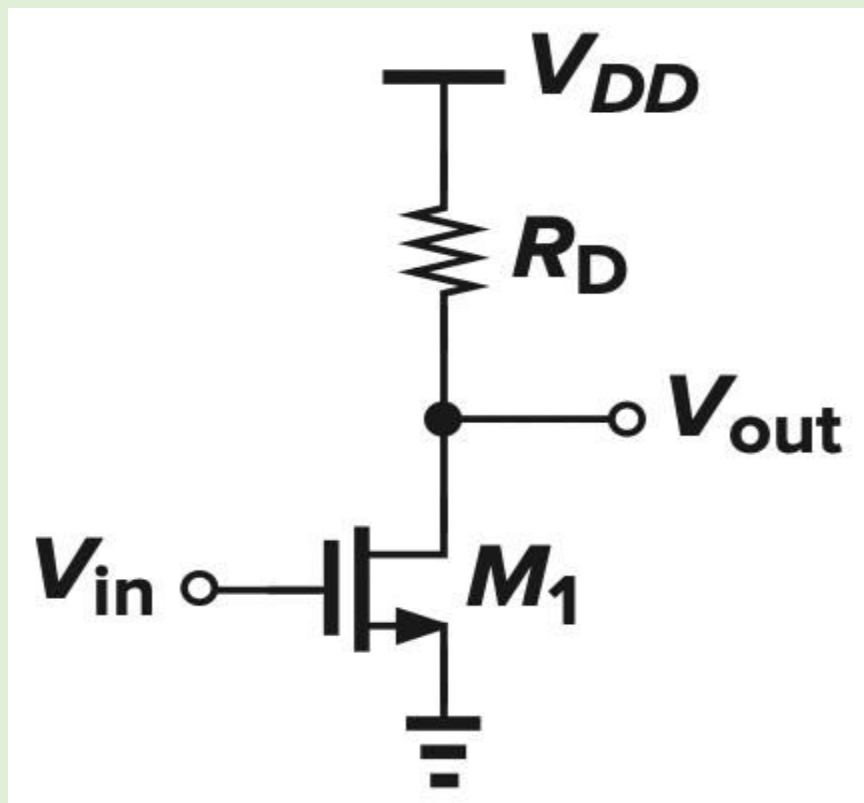

GPT4V:

Type: Common Source Amplifier with NMOS Transistor


Function: This circuit is an electronic amplifier that uses an NMOS transistor as the active device. The input voltage signal (V_{in}) is applied to the gate of the transistor (M_1), and the output voltage (V_{out}) is taken from the drain. The resistor (R_D) serves as the load in the circuit. The common source amplifier configuration provides voltage amplification: the output voltage is an amplified inverted version of the input voltage. The transistor operates in the saturation region when used as an amplifier, acting as a controlled current source driven by the input voltage. This configuration is widely used in analog circuits, especially in applications where a high input impedance is beneficial and some gain is needed.

Library Construction

Prompt:

You are a professional analog circuit engineer. Please identify the type of this subcircuit and reply in the following format:

Type:

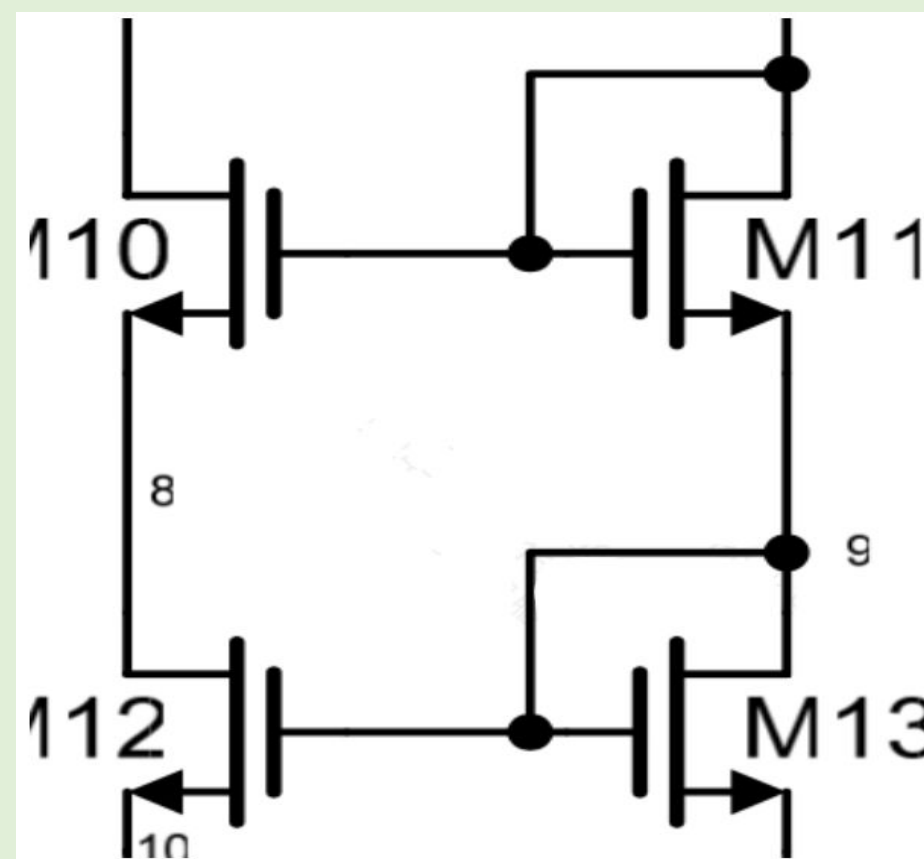

GPT4V:

Type: Cascode Current Mirror

Construct library:

class: Load

netlist:

```
.SUBCKT CASCODE_CURRENT_MIRROR 6 7 10 11
M10 6 7 8 8 nch w=1u h=1u
M11 7 7 9 9 nch w=1u h=1u
M12 8 9 10 10 nch w=1u h=1u
M13 9 9 11 11 nch w=1u h=1u
.ENDS
```

Subcircuit library



Circuit Design

Prompt:

As a professional analog integrated circuit engineer, you are tasked with designing an operational amplifier that meets the following performance criteria:

- High gain
- Wide bandwidth

For each of the following categories, select a subcircuit that best fits the required performance criteria:

Differential pair:

- PMOS differential pair
- NMOS differential pair

Load:

- Resistor
- Diode-connected
- Current mirror
- Folded cascode
- Wilson current mirror
- Widlar current mirror
- Telescopic cascode

Provide a netlist in SPICE format.

GPT4V:

Given the criteria for high gain and wide bandwidth, the NMOS differential pair and folded cascode are ideal subcircuits. Here is an example of a SPICE netlist for an operational amplifier that uses these blocks:

* Power Supply
VDD Vdd GND 5V
VEE Vee GND -5V

* Bias Voltage for differential pair and cascodes
VBias1 Bias1 GND 1.2
VBias2 Bias2 GND 1.8

* Differential Pair NMOS transistors
M1 Outp Inp GND GND NMOS W=60u L=1u
M2 Outn Inn GND GND NMOS W=60u L=1u

* Current Source for the Differential Pair
Ibias Bias1 GND 100uA

* Folded Cascode Load PMOS transistors
M3 Cascp Outp Bias2 Vdd PMOS W=60u L=1u
M4 Cascn Outn Bias2 Vdd PMOS W=60u L=1u

* Folded Cascode NMOS transistors
M5 Cascp Outp Bias1 GND NMOS W=60u L=1u
M6 Cascn Outn Bias1 GND NMOS W=60u L=1u

* Output Stage - Simple current mirror for illustration
M7 Vout Outp Vdd Vdd NMOS W=120u L=1u
M8 Vout Outn GND GND NMOS W=120u L=1u

* Load Resistance (Not part of the Op-Amp, for testing)
RLoad Vout GND 10k

* Differential Input Voltage Sources
Vin_p Inp GND DC 0 AC 1
Vin_n Inn GND DC 0 AC 1

Select subcircuits only.

GPT4V:

Given the performance criteria of high gain and wide bandwidth for an operational amplifier, let's select suitable subcircuits:

Differential Pair: For high gain and wide bandwidth, the differential pair should be able to provide high transconductance and good frequency response. Here are the choices and the reasoning:

PMOS Differential Pair: Typically has lower noise but slower because of the lower electron mobility. It might be used for low-noise applications but might not be the best choice for wide bandwidth requirements.

NMOS Differential Pair: Generally provides higher transconductance and faster operation due to higher electron mobility compared to holes in PMOS devices. This makes the NMOS differential pair a better choice for achieving wide bandwidth.

Selection: **NMOS Differential Pair**

Load: The load of the differential amplifier significantly affects both the gain and the bandwidth. Here are the options and their suitability:

Current Mirror: Provides a constant current, which can help improve linearity and gain, but it might not offer the best output resistance for high gain applications.

...

Selection: **Folded Cascode**

The NMOS differential pair combined with the folded cascode load would be a strong candidate for achieving both high gain and wide bandwidth in the design of an operational amplifier.

Select subcircuit netlists from library to generate circuit

```
*SPICE NETLIST FOR OPAMP
X1 2 3 5 6 FOLDED_CASCODE
X2 2 3 11 12 13 NMOS_DIFF_PAIR
M11 11 14 0 0 NMOS W=1U L=1U
.ENDS
```

```
.SUBCKT FOLDED_CASCODE 2 3 5 6
M1 2 1 VDD VDD PMOS W=1U L=1U
M2 3 1 VDD VDD PMOS W=1U L=1U
M3 5 4 2 VDD PMOS W=1U L=1U
M4 6 4 3 VDD MOS W=1U L=1U
M5 5 7 8 0 NMOS W=1U L=1U
M6 6 7 9 0 NMOS W=1U L=1U
M7 8 10 0 0 NMOS W=1U L=1U
M8 9 10 0 0 NMOS W=1U L=1U
.ENDS
```

```
.SUBCKT NMOS_DIFF_PAIR 2 3 11 12 13
M9 2 12 11 0 NMOS W=1U L=1U
M10 3 13 11 0 NMOS W=1U L=1U
.ENDS
```

Human evaluation:

Despite generating a decent list of components, the connectivity appear incorrect overall.



Human evaluation:

The current state of art MLLM seems capable of selecting the correct sub-blocks.

